



East West University  
Department of Computer Science and Engineering

Course: CSE345 Digital Logic Design

Expt No.: 2

Title: Design and Implementation of a Combinational Circuit

**Objectives:**

1. To design a combinational circuit from descriptive problem specification.
2. To implement a combinational circuit using AND-OR and OR-AND logic.

**Theory:**

The design procedure of a combinational circuit is discussed in Section 6.2 of Textbook 1. Students are advised to go through the above section of the Textbook 1 before preparing the pre-lab report.

**Pre-Lab Report Questions:**

**Problem specification:** In a combinational logic circuit, four input lines  $A$ ,  $B$ ,  $C$ , and  $D$  are being used to represent a 4-bit binary number with  $A$  as the MSB and  $D$  as the LSB. The circuit produces a high (logic 1) output only when the binary number is greater than 0101.

1. Prepare a truth table for the given combinational circuit. Represent the truth table in a 4-variable K-map.
2. Write simplified sum of products function from the K-map. Draw the AND-OR logic diagram for the simplified sum of products function.
3. Write simplified product of sums function from the K-map. Draw OR-AND logic diagram for the simplified product of sums function.


**ICs Required:**

7408 Quadruple 2-input AND gates

7432 Quadruple 2-input OR gates


**Pin Diagram of the Required ICs:**

1	1A	14	1	1A	14
2	1B	13	2	1B	13
3	1Y	12	3	1Y	12
4	2A	11	4	2A	11
5	2B	10	5	2B	10
6	2Y	9	6	2Y	9
7	GND	8	7	GND	8
7408 (4 2-In AND)			7432 (4 2-In OR)		


 


truth table:


ABCD	F
0000	0
0001	0
0010	0
0011	0
0100	0
0101	0
0110	1
0111	1
1000	1
1001	1
1010	1
1011	1
1100	1
1101	1
1110	1
1111	1

 

$$F = A + Bc$$

  

$$F = (A+B)(A+c)$$

 



East West University  
Department of Computer Science and Engineering

Course: CSE345 Digital Logic Design

Expt No.: 4

Title: Binary Adder and Subtractor

Objectives:

1. To implement and test a full adder using discrete gates.
1. To implement and test a 4-bit 2's complement adder/subtractor using IC 7483 (4-bit binary parallel adder).

Theory:

Design of full-adder using discrete gates is discussed in Section 7.2 of textbook. The IC 7483 (4-bit binary parallel adder) is introduced in Section 7.8 of textbook. Design of a 4-bit 2's complement adder/subtractor using a 4-bit binary parallel adder is discussed in Section 7.6 of textbook.

Pre-Lab Report Questions:

Implementing and testing a full adder using discrete gates:

1. Draw the logic diagram of a full-adder using EXOR gates.
2. Write the truth table of a full-adder.

Implementing and testing a 4-bit 2's complement adder/subtractor using IC 7483 (4-bit binary parallel adder):

3. Draw the schematic diagram for implementing a 4-bit 2's complement adder/subtractor using IC 7483 (4-bit binary parallel adder). Write the operation of the circuit explaining how the mode selector input  $M$  determines the mode of operations as adder or subtractor.

2's complement addition and subtraction:

4. Perform the following 2's complement additions and subtractions using 4-bit data: লিখ আরও হবে।

$3 + 3$	$3 - 2$
$3 + 4$	$3 - 3$
$3 + 5$ (overflow)	$3 - 4$

ICs Required:

7408 Quadruple 2-input AND gates  
7432 Quadruple 2-input OR gates  
7486 Quadruple 2-input EXOR gates  
7483 4-bit binary parallel adder

Pin Diagram of the Required ICs:

7408 (4 2-Input AND)			7432 (4 2-Input OR)			7486 (4 2-Input EXOR)		
1	1A	V <sub>CC</sub>	1	1A	V <sub>CC</sub>	1	1A	V <sub>CC</sub>
2	1B	4B	2	1B	4B	2	1B	4B
3	1Y	4A	3	1Y	4A	3	1Y	4A
4	2A	4Y	4	2A	4Y	4	2A	4Y
5	2B	3B	5	2B	3B	5	2B	3B
6	2Y	3A	6	2Y	3A	6	2Y	3A
7	GND	3Y	7	GND	3Y	7	GND	3Y
14			14			14		

8	7	6	5	4	3	2	1
A <sub>1</sub>	B <sub>1</sub>	S <sub>1</sub>	V <sub>CC</sub>	B <sub>2</sub>	A <sub>2</sub>	S <sub>2</sub>	A <sub>3</sub>
7483							
S <sub>0</sub>	A <sub>0</sub>	B <sub>0</sub>	GND	C <sub>0</sub>	C <sub>1</sub>	S <sub>3</sub>	B <sub>3</sub>
9	10	11	12	13	14	15	16

#### Lab Procedure:

##### Implementing and testing a full adder using random gates:

- Construct the logic diagram for a full-adder from your pre-lab report on the breadboard. Connect the three inputs of the circuit to three data switches and two outputs to two LED indicators.
- Show the outputs of the circuit to your instructor.

##### Implementing and testing a 4-bit 2's complement adder/subtractor using IC 7483 (4-bit binary parallel adder):

- Construct the schematic diagram for a 4-bit 2's complement adder/subtractor using IC 7483 from your pre-lab report. Connect the four A inputs to a fixed binary number 0011 (decimal 3) to two data switches and the four B inputs to four data switches. Connect the mode select input M to a data switch. Connect the four sum outputs S and carry output C<sub>4</sub> to five LED indicators.
- Perform the following addition/subtraction operations.

3 + 3	3 - 2
3 + 4	3 - 3
3 + 5 (overflow)	3 - 4


- Show the outputs of the circuit to your instructor.

#### Post-Lab Report Questions:

- Write structural Verilog code for full-adder circuit from your pre-lab report and simulate it using Quartus II software.
- Write behavioral Verilog code for a 4-bit parallel adder and simulate it using Quartus II software.



## Pin Diagram of 74283

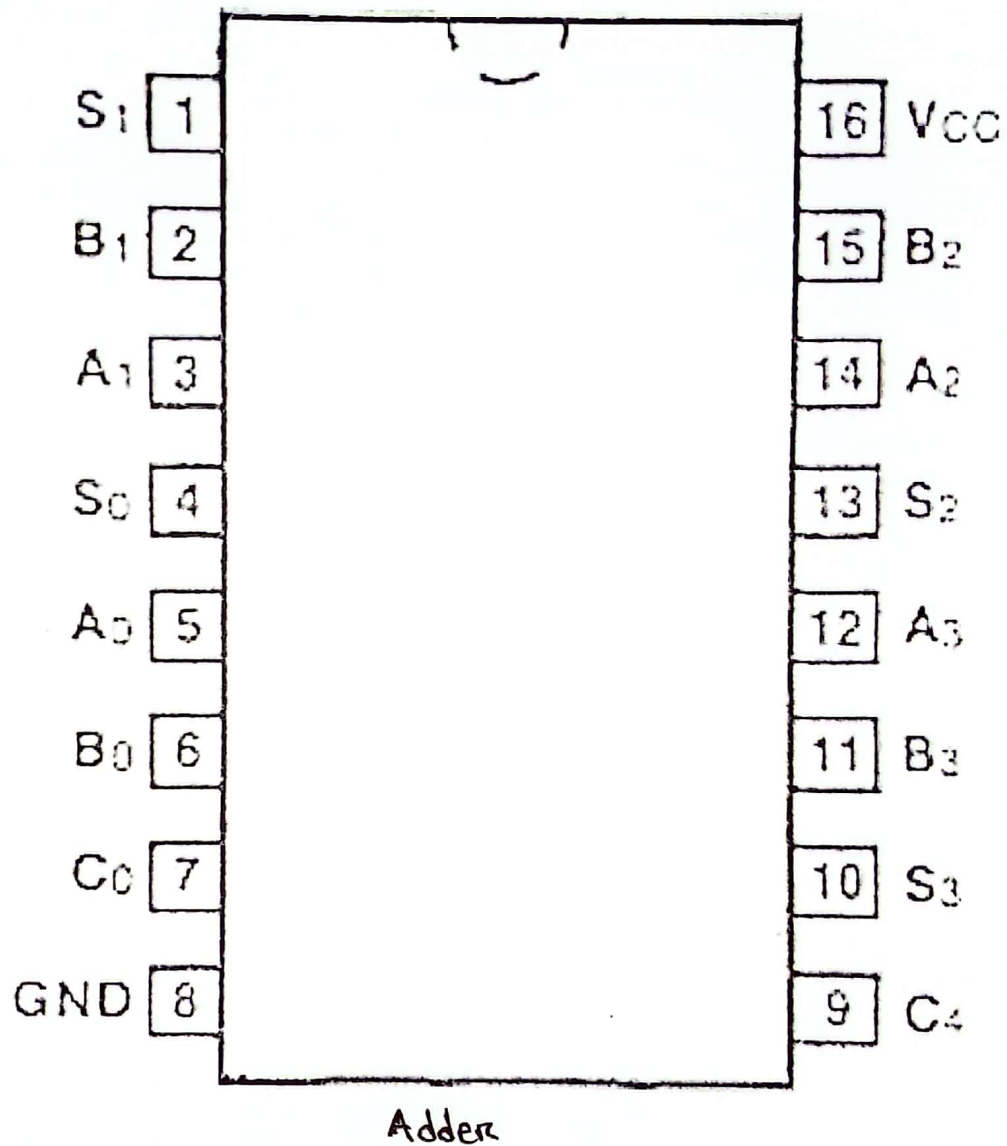

Exp-1

4. Perform the following 2's complement additions and subtractions using 4-bit data:

✓ i.  $3+3$

$$\begin{array}{r} +3 \rightarrow 0011 \\ +3 \rightarrow 0011 \\ \hline +6 \rightarrow 0110 \end{array}$$

ii)  $+3+4$

$$\begin{array}{r} +3 \rightarrow 0011 \\ +4 \rightarrow 0100 \\ \hline +7 \rightarrow 0111 \end{array}$$

✓ iii)  $3+5$

$$\begin{array}{r} +3 \rightarrow 0011 \\ +5 \rightarrow 0101 \\ \hline +8 \rightarrow 1000 \text{ [overflow]} \\ (-8)_{10} \rightarrow (1000)_2 \end{array}$$

✓ iv)  $3-2$

$$= 3 + (-2)$$

$$2 \rightarrow 0010 \xrightarrow{2's} 1110 = (-2)$$

$$\begin{array}{r} +3 \rightarrow 0011 \\ -2 \rightarrow 1110 \\ \hline +1 \rightarrow 10001 \\ \text{Discard} \end{array}$$

249840

$$v) 3-3$$

$$= 3 + (-3)$$

$$3 \rightarrow 0011 \xrightarrow{2's} 1101 = (-3)$$

$$+3 \rightarrow 0011$$

$$-3 \rightarrow 1101$$

$$\begin{array}{r} 0011 \\ + 1101 \\ \hline 10000 \\ \text{Discard} \end{array}$$

$$vi) 3-4$$

$$= 3 + (-4)$$

$$4 \rightarrow 0100 \xrightarrow{2's} 1100 = (-4)$$


$$+3 \rightarrow 0011$$

$$-4 \rightarrow 1100$$

$$\begin{array}{r} 0011 \\ + 1100 \\ \hline 1111 \end{array}$$

$$A_i \oplus B_i \oplus C_i$$


$$S_i = (A_i \oplus B_i) C_i + A_i B_i$$

 

Truth table:

$A_i$	$B_i$	$C_i$	$C_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



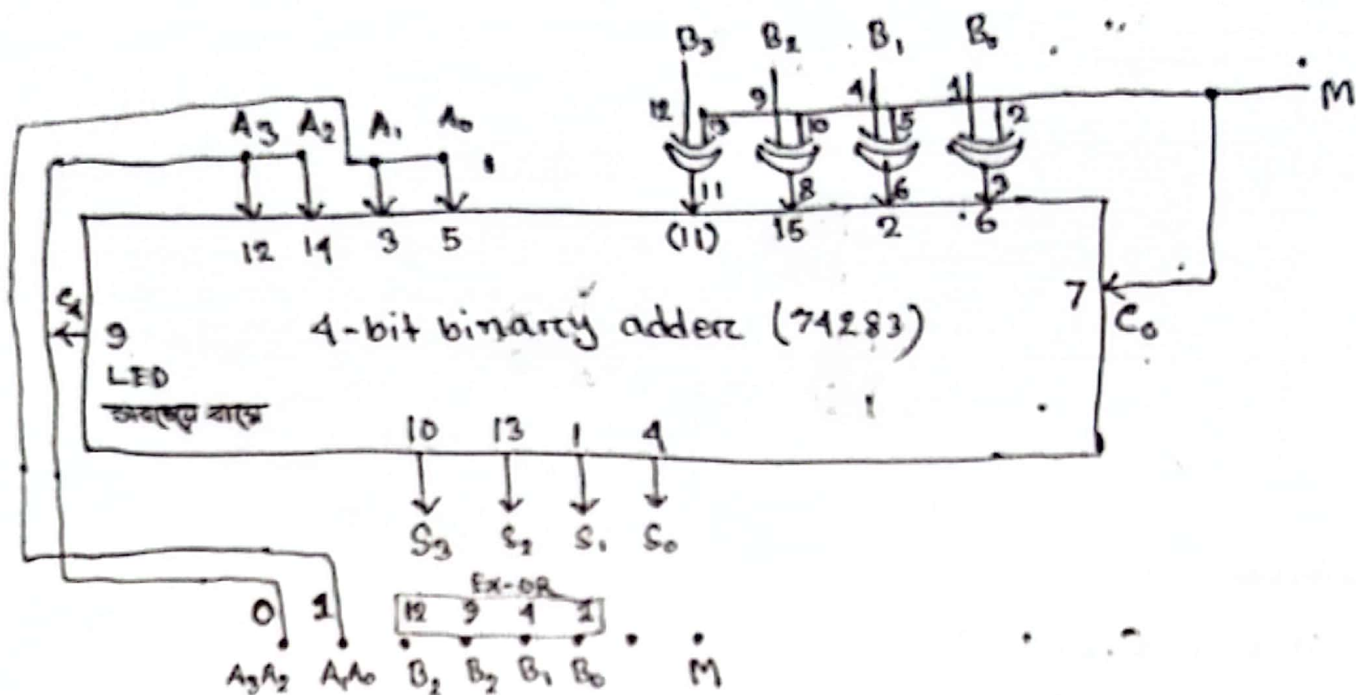



East West University  
Department of Computer Science and Engineering

Course: CSE345 Digital Logic Design

Expt No.: 5

Title: Decoder and Its Use in Combinational Logic Implementation

**Objectives:**

- ✓ 1. To implement and test a 2-to-4-lines decoder with active-LOW outputs and active-LOW enable input using random gates.
1. To implement and test combinational logic functions using IC 74138 (3-to-8-lines decoder with active-LOW outputs).

**Theory:**

Design of decoders using random gates is discussed in Section 8.3 of textbook 1. The IC 74138 (3-to-8-line decoder with active-LOW outputs) is introduced in Section 8.3 of textbook 1. Combinational logic implementation using decoders is also discussed in Section 8.3 of textbook 1.

**Pre-Lab Report Questions:**

Implementing and testing a 2-to-4-lines decoder with active-LOW outputs and active-LOW enable input using random gates:

- ✓ 1. Draw the logic diagram for a 2-to-4-lines decoder with active-LOW outputs and active-LOW enable input.
- ✓ 2. Write the truth table of the above decoder.

Implementing and testing combinational logic functions using the IC 74138 (3-to-8-lines decoder with active-LOW outputs):

3. Draw the schematic diagram for implementing the following two combinational logic functions using the IC 74138 (3-to-8-lines decoder with active-LOW outputs).

$$F_1(A, B, C) = \sum(1, 2, 4, 7)$$

$$F_2(A, B, C) = \sum(0, 5, 6, 7)$$

Binary Bit হিসেবে Input দিচ্ছো।

**ICs Required:**

- 7404 Hex Inverters (NOT gates)
- 7410 Triple 3-input NAND gates
- 7420 Dual 4-input NAND gates
- 74138 3-to-8-line decoder with active-LOW outputs

**Pin Diagram of the Required ICs:**

**Pin Diagram of the Required ICs:**

Pin	1A	U	V <sub>CC</sub>
1	1A	U	V <sub>CC</sub>
2	1Y	6A	13
3	2A	6Y	12
4	2Y	5A	11
5	3A	5Y	10
6	3Y	4A	9
7	GND	4Y	8

7404 (6 NOT)

Pin	1A	U	V <sub>CC</sub>
1	1A	U	V <sub>CC</sub>
2	1B	1C	13
3	2A	1Y	12
4	2B	3C	11
5	2C	3B	10
6	2Y	3A	9
7	GND	3Y	8

7410 (3 3-In NAND)

Pin	1A	U	V <sub>CC</sub>
1	1A	U	V <sub>CC</sub>
2	1B	2D	13
3	NC	2C	12
4	1C	NC	11
5	1D	2B	10
6	1Y	2A	9
7	GND	2Y	8

7420 (2 4-In NAND)

→ No connection.

16	15	14	13	12	11	10	9
$V_{CC}$	$O_0$	$O_1$	$O_2$	$O_3$	$O_4$	$O_5$	$O_6$
74138							
$A_0$	$A_1$	$A_2$	$E_1$	$E_2$	$E_3$	$O_7$	GND
1	2	3	4	5	6	7	8

## Decoder

4, 5 number থেকে কতটা 0 input  
6 " " " 1 input " "

### Lab Procedure:

Lab Procedure:  
Implementing and testing a 2-to-4-lines decoder with active-LOW outputs and active-LOW enable input using random gates:

1. Construct the logic diagram for a 2-to-4-lines decoder with active-LOW outputs and active-LOW enable input from your pre-lab report using random gates. Connect the three inputs ( $A_1$ ,  $A_0$ , and  $E$ ) of the circuit to three data switches and four outputs to four LED indicators.
2. Apply binary 00 to 11 to  $A_1A_0$  address inputs and observe the outputs by changing  $E$  enable input. Verify the operation.

**Implementing and testing combinational logic functions using the IC 74138 (3-to-8-lines decoder with active-LOW outputs):**

3. Construct the circuits for implementing the given combinational logic functions from your pre-lab report. Connect enable inputs  $E_1$  and  $E_2$  to fixed 0s and  $E_3$  to a data switch. Use  $E_3$  as active-HIGH enable input. Connect the input lines  $ABC$  ( $A_2A_1A_0$ ) to three data switches. Connect the two function outputs to two LED indicators.
4. Prepare the truth tables of the circuit and verify that it implements the two given combinational logic functions.


### Post-Lab Report Questions:

1. Verify that all experimental outputs agree with your pre-lab report.
2. Write structural Verilog code for the logic diagram for a 2-to-4-lines decoder with active-LOW outputs and active-LOW enable input from your pre-lab report and simulate it using Quartus II software.
3. Write behavioral Verilog code for 3-to-8-lines decoder with active-LOW outputs and simulate it using Quartus II software.

Ver: 2 to 4

Adder-Subtractor - 18  
Encoder-decoder - 28

 Active-Low Enable Input and Active Low outputs.



Inputs			Outputs			
E	A <sub>1</sub>	A <sub>0</sub>	O <sub>3</sub>	O <sub>2</sub>	O <sub>1</sub>	O <sub>0</sub>
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1


$$O_0 = E + A_1 + A_0 = (E'A_1'A_0)'$$

$$O_1 = E + A_1 + A_0' = (E'A_1'A_0')'$$


$$O_2 = E + A_1' + A_0 = (E'A_1'A_0)'$$

$$O_3 = E + A_1' + A_0' = (E'A_1'A_0')'$$

\* 3 input का 2 नान्ड Ie लगाए

 

 Output  
O<sub>3</sub> O<sub>2</sub> O<sub>1</sub> O<sub>0</sub>






Decoder দিয়ে Function Implementation:

$$F_1(A, B, C) = \Sigma(1, 2, 4, 7)$$

$$F_2(A, B, C) = \Sigma(0, 5, 6, 7)$$

 

4 input NAND লাগবে।

Decoder এর 14 থেকে NAND এর 1  
 " " 13 " NAND " 2  
 " " 11 " " " 4  
 " " 7 " " " 5

$E_3, E_4$  জট করে 0-তে connect  
 করতে হবে।

3 2 1  
 • • •  
 A B C  
 A<sub>2</sub> A<sub>1</sub> A<sub>0</sub>

Decoder এ ফাংশন  
 Fixed হবে।





East West University  
Department of Computer Science and Engineering

Course: CSE345 Digital Logic Design

Expt No.: 6

Title: Multiplexer and Its Use in Combinational Logic Implementation

**Objectives:**

1. To implement and test a 4-to-1-line multiplexer with active-LOW enable input using random gates.
2. To implement and test combinational logic function using IC 74151 (8-to-1-line multiplexer with active-LOW enable input).

**Theory:**

Design of multiplexers using random gates is discussed in Section 8.7 of textbook 1. The IC 74151 (8-to-1-line multiplexer with active-LOW enable input) is introduced in Section 8.7 of textbook 1. Combinational logic implementation using multiplexers is also discussed in Section 8.7 of textbook 1.

**Pre-Lab Report Questions:**

Implementing and testing a 4-to-1-line multiplexer with active-LOW enable input using random gates:

1. Write the truth table of a 4-to-1-line multiplexer with active-LOW enable input.
2. Draw the logic diagram of a 4-to-1-line multiplexer with active-LOW enable input using random gates.

Implementing and testing combinational logic function using IC 74151 (8-to-1-line multiplexer with active-LOW enable input):

3. Prepare the implementation table for implementing the combinational logic function  $F(A, B, C, D) = \sum(0, 3, 4, 6, 8, 11, 13, 15)$  using an 8-to-1-line multiplexer.
4. Draw the logic diagram for implementing the above logic function using IC 74151 (8-to-1-line multiplexer with active-LOW enable input).

**ICs Required:**

7404 Hex Inverters (NOT gates)  
7421 Double 4-input AND gates  
7432 Quadruple 2-input OR gates  
74151 8-to-1-line multiplexer with active-LOW enable input

### Pin Diagram of the Required ICs:

1	1A	V <sub>CC</sub>	14	1	1A	V <sub>CC</sub>	14	1	1A	V <sub>CC</sub>	14
2	1Y	6A	13	2	1B	2D	13	2	1B	4B	13
3	2A	6Y	12	3	NC	2C	12	3	1Y	4A	12
4	2Y	5A	11	4	1C	NC	11	4	2A	4Y	11
5	3A	5Y	10	5	1D	2B	10	5	2B	3B	10
6	3Y	4A	9	6	1Y	2A	9	6	2Y	3A	9
7	GND	4Y	8	7	GND	2Y	8	7	GND	3Y	8

7404 (6 NOT)

7421 (2 4-In AND)

7432 (4 2-In OR)

16	15	14	13	12	11	10	9
V <sub>CC</sub>	I <sub>4</sub>	I <sub>5</sub>	I <sub>6</sub>	I <sub>7</sub>	A <sub>0</sub>	A <sub>1</sub>	A <sub>2</sub>
74151							
I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>	O	O	EGND	
1	2	3	4	5	6	7	8

### Lab Procedure:

**Implementing and testing a 4-to-1-line multiplexer with active-LOW enable input using random gates:**


1. Construct the logic diagram for a 4-to-1-line multiplexer with active-LOW enable input from your pre-lab report using random gates. Connect the four data inputs  $I_0$  through  $I_3$  to an arbitrary 4-bit binary number. Connect  $A_1$ ,  $A_0$ , and  $E$  to three switches and the output  $O$  to an LED indicator.
2. Apply binary 00 to 11 to address lines  $A_1A_0$  and observe the outputs by changing  $E$  input. Check that, when the circuit is enabled, the output is equal to the selected data input. Prepare the observed truth table indicating the inputs applied.

**Implementing and testing combinational logic function using IC 74151 (8-to-1-line multiplexer with active-LOW enable input):**


3. Construct the logic diagram for implementing the logic function  $F(A, B, C, D) = \sum(0, 3, 4, 6, 8, 11, 13, 15)$  from your pre-lab report using IC 74151 (8-to-1-line multiplexer with active-LOW enable input).
4. Prepare the truth table of the circuit and verify that it implements the given combinational logic function.

### Post-Lab Report Questions:

 1. Verify that all experimental outputs agree with your pre-lab report.
2. Write structural Verilog code for the logic diagram for a 4-to-1-line multiplexer with active-LOW enable input from your pre-lab report and simulate it using Quartus II software.
3. Write behavioral Verilog code for a 4-to-1-line multiplexer with active-LOW enable input and simulate it using Quartus II software.



E	A <sub>1</sub>	A <sub>0</sub>	O
0	0	0	I <sub>0</sub>
0	0	1	I <sub>1</sub>
0	1	0	I <sub>2</sub>
0	1	1	I <sub>3</sub>
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 

$$F = I_0 E' A_1' A_0' + I_1 E' A_1' A_0 + I_2 E' A_1 A_0' + I_3 E' A_1 A_0$$


$\dot{E} \dot{A}_1 \dot{A}_0 \dot{I}_0 \dot{I}_1 \dot{I}_2 \dot{I}_3$   
(উচ্চের Not  
ব্যবহৃত হবে)

\* 000 নিনে I<sub>0</sub> select হবে এছাড়া I<sub>0</sub> কে 1 ব্যবহৃত হবে। I<sub>0</sub> = 1 দিনে LED জ্বলবে।

\*  $F(A, B, C, D) = \Sigma (0, 3, 4, 6, 8, 11, 13, 15)$  এগুলো জন্ম LED জ্বলবে।

Implementation table:

A'	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	0	0	1	A'	A	A'	A

 

0000  
0001  
0010  
0011  
0100  
0101  
0110  
0111  
1000  
1001  
1010  
1011  
1100  
1101  
1110  
1111